

**Q1.** (a) For the Boolean expression given below

$$F(A,B,C,D) = \sum m(3,4,5, 8,11,15)$$

$$d(A,B,C,D) = \sum m(0,2,9)$$

- (i) Plot the k-Map
  - (ii) Identify the Prime Implicants. Express each PI as product form.
  - (iii) Identify the essential Prime Implicants. Express each EPI as product form.
  - (iv) How many different minimal SOPs are possible for F? Write down the expression for all the minimal SOP for F.
  - (v) Draw the gate level circuit diagram of the minimal SOP (any one) using required number of two input NAND gates.
- (b) Express the following function as sum of minterms and product of maxterms.

$$F(A,B,C,D) = B'D + A'D + BD$$

**Q2.** Realize the following four variable function using minimum number of 2:1 MUXs only. NO other gates/components are available. Also only true forms of input variables are available.

$$F = AB + B'CD + AC'$$

**Q3. (a)** Implement the following Boolean function using minimum number of

- (i) Transistors in CMOS logic
- (ii) Transmission gates & NOT gates.

$$F(A,B,C) = A'B' + (B+C)' + ABC$$

Assume inputs available in true and compliment forms.

**(b)** Mention any two merits and demerits of TTL totem-pole over TTL Open collector logic family