

Transmission Lines as circuit elements


For a lossless line:

$$Z_{in} = Z_o \left[\frac{Z_L + jZ_o \tan \beta l}{Z_o + jZ_L \tan \beta l} \right]$$


Transmission Lines terminated in short or open circuits are commonly used as tuning elements.

If the line is **short-circuited**: $Z_L = 0$

$$Z_{sc} = jZ_o \tan \beta l$$

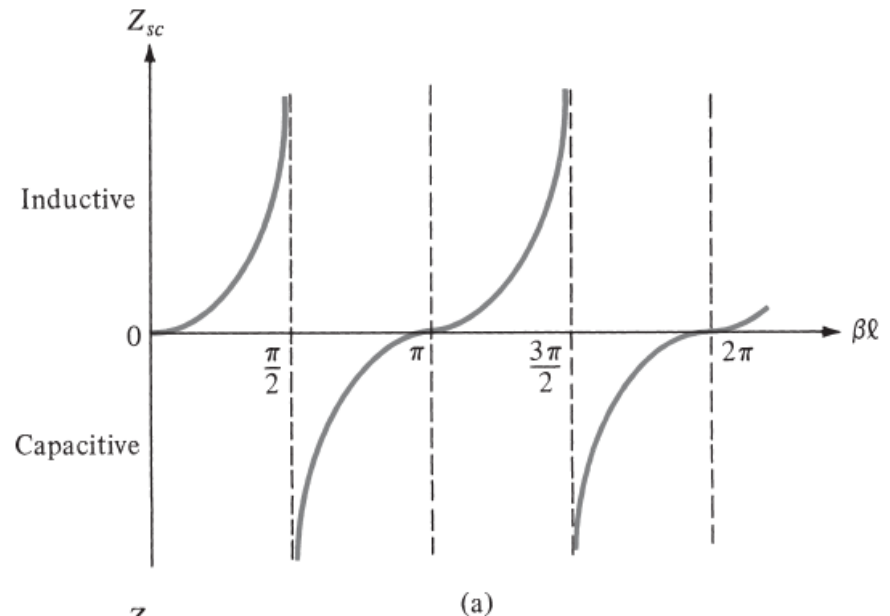

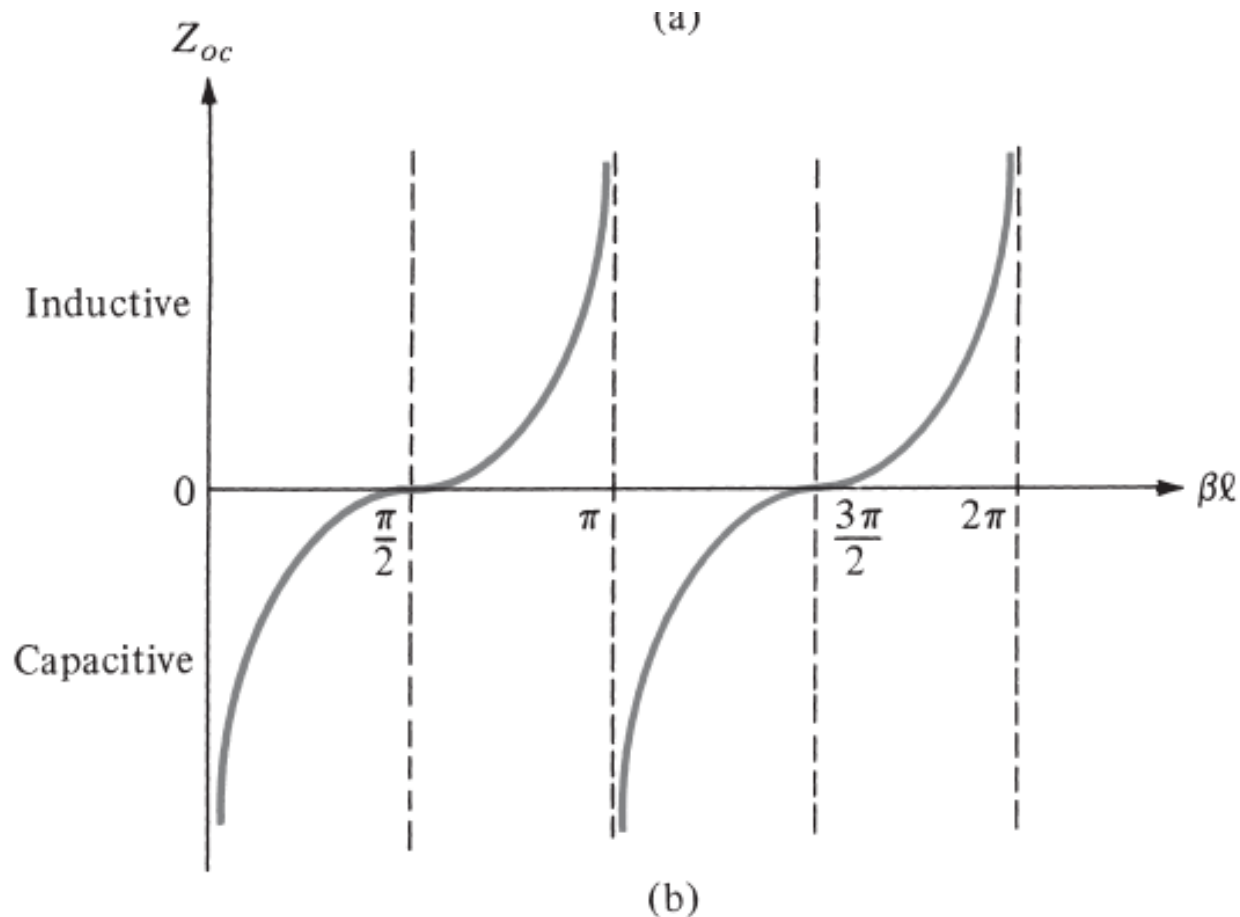For a lossless line: **open-circuited**: $Z_L = \text{infinity}$



$$Z_{in} = -jZ_o \cot \beta l$$

$$Z_o = \sqrt{Z_{oc} Z_{sc}}$$

$$\gamma = \frac{1}{l} \tanh^{-1} \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$


Short television antenna lead-in wire

- The open-circuit and short-circuit impedances measured at the input terminals of a TV antenna lead-in wire of length 1.5 (m), which is less than a quarter wavelength, are $-j54.6$ ohm and $j103$ ohm, respectively. (a) Find Z_0 and propagation constant of the line. (b) Without changing the operating frequency, find the input impedances of a short-circuited line that is twice the given length.
- **Answers:** (a) 75 ohm, $j0.628$ rad/m; (b) $-j231$ ohm

SMITH CHART

- Transmission line calculation-such as the determination of input impedance, reflection coefficient and load impedance often involve tedious manipulations of complex numbers.
- Graphical method of solution → **Smith Chart**
- **Smith Chart** was devised by P.H.Smith (in 1930).
- Smith Chart is a graphical plot of normalized resistance and reactance functions in the reflection-coefficient plane

Introduction

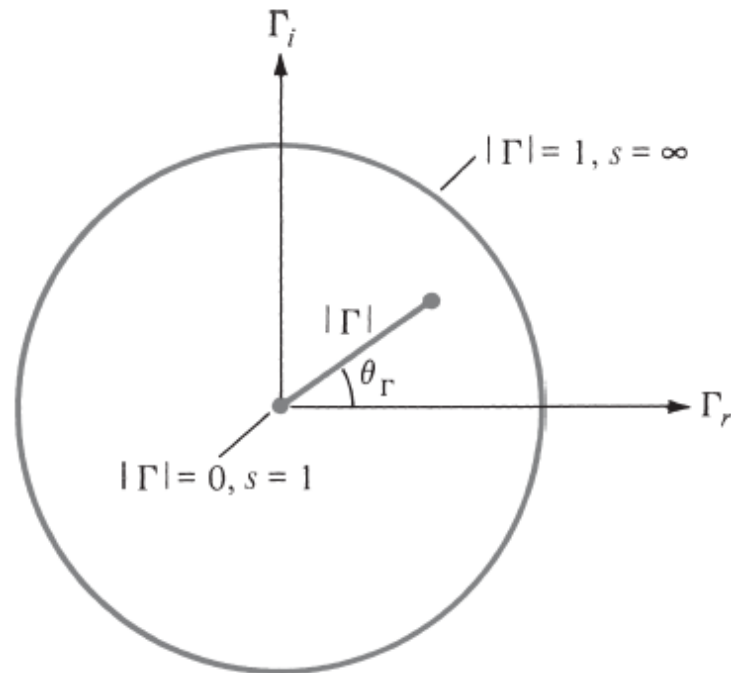

The **normalized impedance** is represented on the **Smith chart** by using families of curves that identify the **normalized resistance r** (real part) and the **normalized reactance x** (imaginary part)

- If a lossless line of Z_0 is terminated with Z_L , $z_L = Z_L/Z_0$ (normalized load impedance),

$$\Gamma = \frac{z_L - 1}{z_L + 1} = |\Gamma| e^{j\theta} \quad \longrightarrow \quad z_L = \frac{1 + |\Gamma| e^{j\theta}}{1 - |\Gamma| e^{j\theta}}$$

- Let $\Gamma = \Gamma_r + j\Gamma_i$, and $z_L = r_L + jx_L$.

$$r_L + jx_L = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} \quad \longrightarrow \quad r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad x_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$\left(\Gamma_r - \frac{r_L}{1 + r_L} \right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L} \right)^2,$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L} \right)^2 = \left(\frac{1}{x_L} \right)^2$$

The **real part** gives

Add a quantity equal to zero

$$r = \frac{1 - \operatorname{Re}^2(\Gamma) - \operatorname{Im}^2(\Gamma)}{(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma)}$$

= 0

$$r(\operatorname{Re}(\Gamma) - 1)^2 + (\operatorname{Re}^2(\Gamma) - 1) + r\operatorname{Im}^2(\Gamma) + \operatorname{Im}^2(\Gamma) + \frac{1}{1+r} - \frac{1}{1+r} = 0$$

$$\left[r(\operatorname{Re}(\Gamma) - 1)^2 + (\operatorname{Re}^2(\Gamma) - 1) + \frac{1}{1+r} \right] + (1+r)\operatorname{Im}^2(\Gamma) = \frac{1}{1+r}$$

$$(1+r) \left[\operatorname{Re}^2(\Gamma) - 2\operatorname{Re}(\Gamma) \frac{r}{1+r} + \frac{r^2}{(1+r)^2} \right] + (1+r)\operatorname{Im}^2(\Gamma) = \frac{1}{1+r}$$

$$\Rightarrow \left[\operatorname{Re}(\Gamma) - \frac{r}{1+r} \right]^2 + \operatorname{Im}^2(\Gamma) = \left(\frac{1}{1+r} \right)^2$$

Equation of a circle

The **imaginary part** gives

Multiply by x and add a quantity equal to zero

$$x = \frac{2 \operatorname{Im}(\Gamma)}{(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma)}$$

$$x^2 \left[(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma) \right] - 2x \operatorname{Im}(\Gamma) + \underbrace{1 - 1}_{=0} = 0$$

$$\left[(1 - \operatorname{Re}(\Gamma))^2 + \operatorname{Im}^2(\Gamma) \right] - \frac{2}{x} \operatorname{Im}(\Gamma) + \frac{1}{x^2} = \frac{1}{x^2}$$

$$(1 - \operatorname{Re}(\Gamma))^2 + \left[\operatorname{Im}^2(\Gamma) - \frac{2}{x} \operatorname{Im}(\Gamma) + \frac{1}{x^2} \right] = \frac{1}{x^2}$$

$$\Rightarrow (\operatorname{Re}(\Gamma) - 1)^2 + \left[\operatorname{Im}(\Gamma) - \frac{1}{x} \right]^2 = \frac{1}{x^2}$$

Equation of a circle


$$\left(\Gamma_r - \frac{r_L}{1+r_L}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r_L}\right)^2,$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2$$

The result for the **real part** indicates that on the complex plane with coordinates $(\text{Re}(\Gamma), \text{Im}(\Gamma))$ all the possible impedances with a given normalized resistance **r** are found on a **circle** with

$$\text{Center} = \left\{ \frac{r}{1+r}, 0 \right\} \quad \text{Radius} = \frac{1}{1+r}$$

As the normalized resistance **r** varies from **0** to **∞** , we obtain a family of circles completely contained inside the domain of the reflection coefficient **$|\Gamma| \leq 1$** .

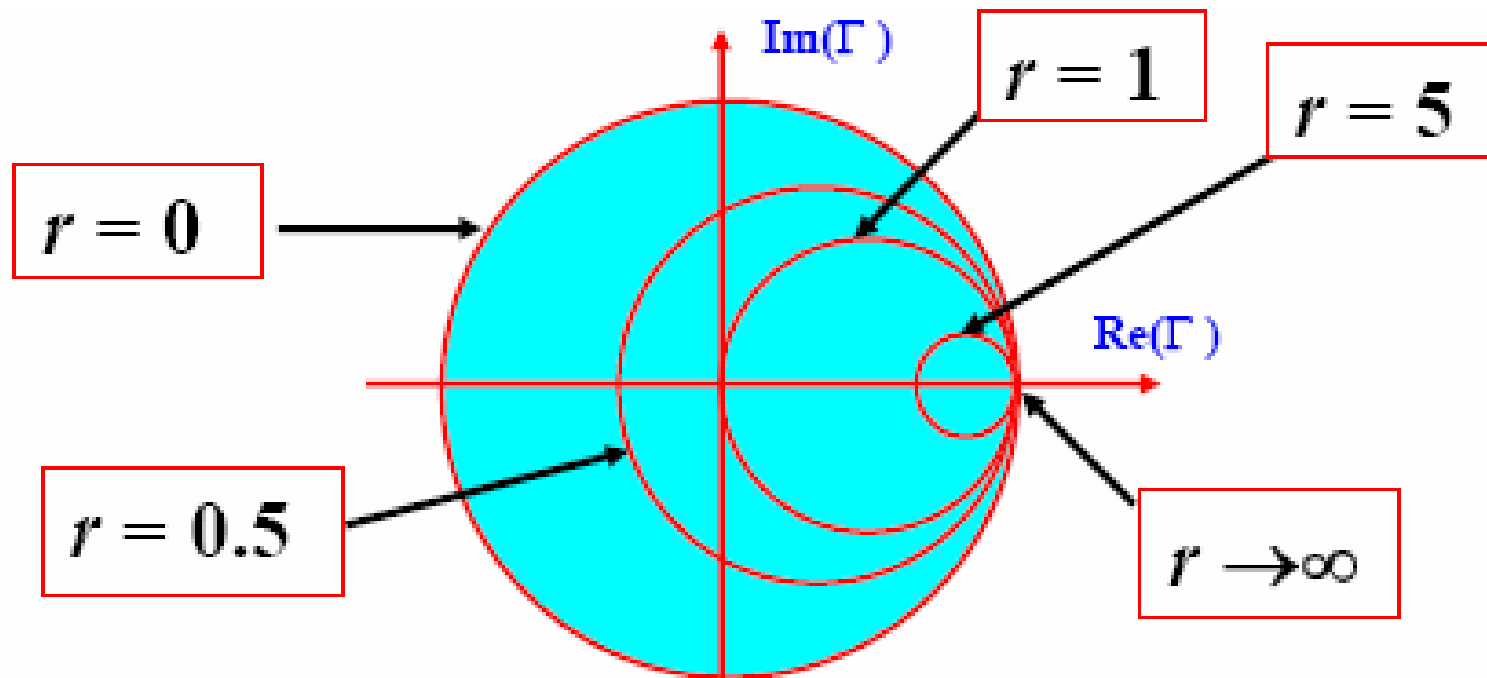


$$\text{Center} = \left\{ \frac{r}{1+r}, 0 \right\}$$

$$\text{Radius} = \frac{1}{1+r}$$


The result for the **imaginary part** indicates that on the complex plane with coordinates $(\text{Re}(\Gamma), \text{Im}(\Gamma))$ all the possible impedances with a given normalized reactance x are found on a **circle** with

$$\text{Center} = \left\{ 1, \frac{1}{x} \right\} \qquad \text{Radius} = \frac{1}{x}$$

As the normalized reactance x varies from $-\infty$ to ∞ , we obtain a family of arcs contained inside the domain of the reflection coefficient $|\Gamma| \leq 1$.

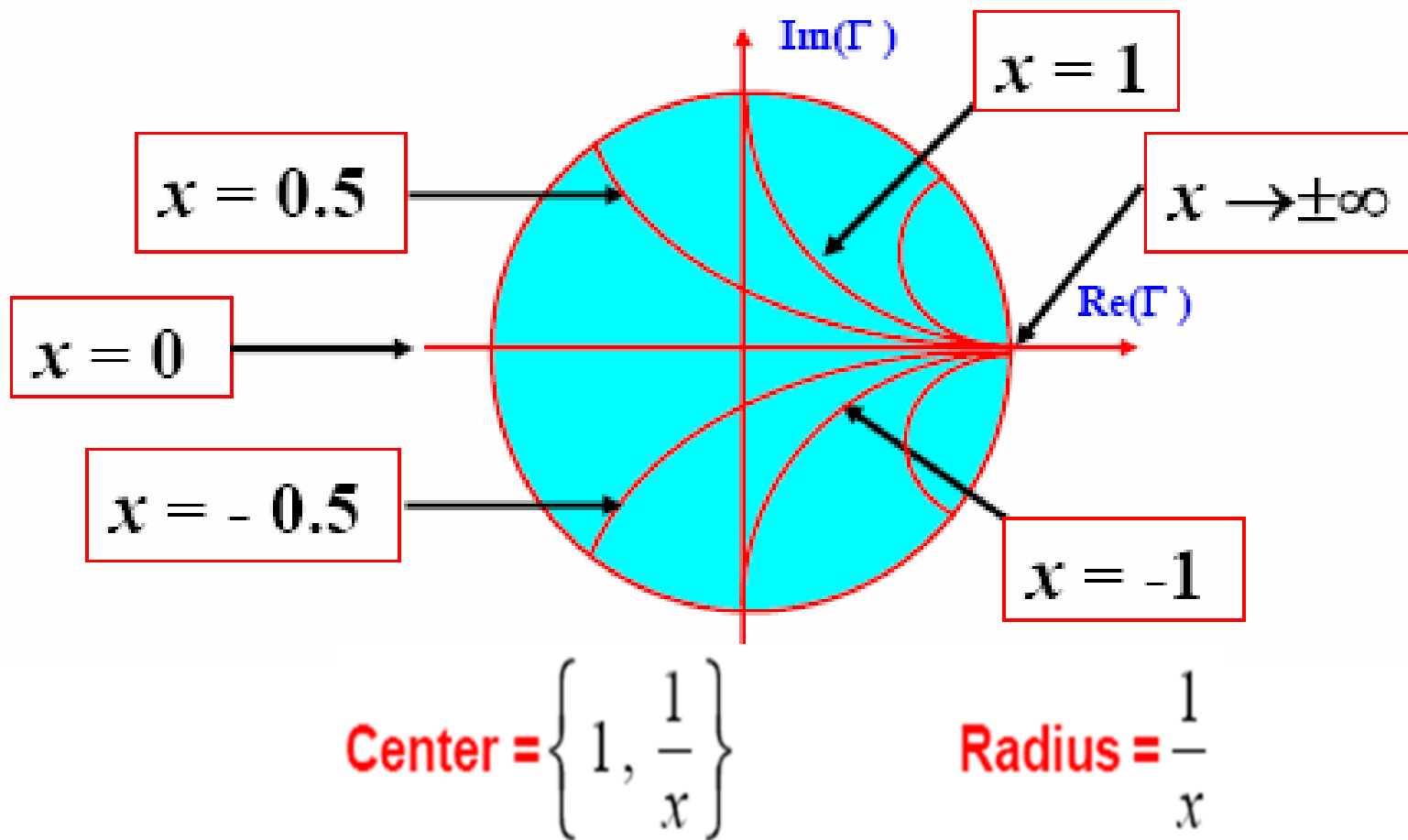


Superimpose the two circles families

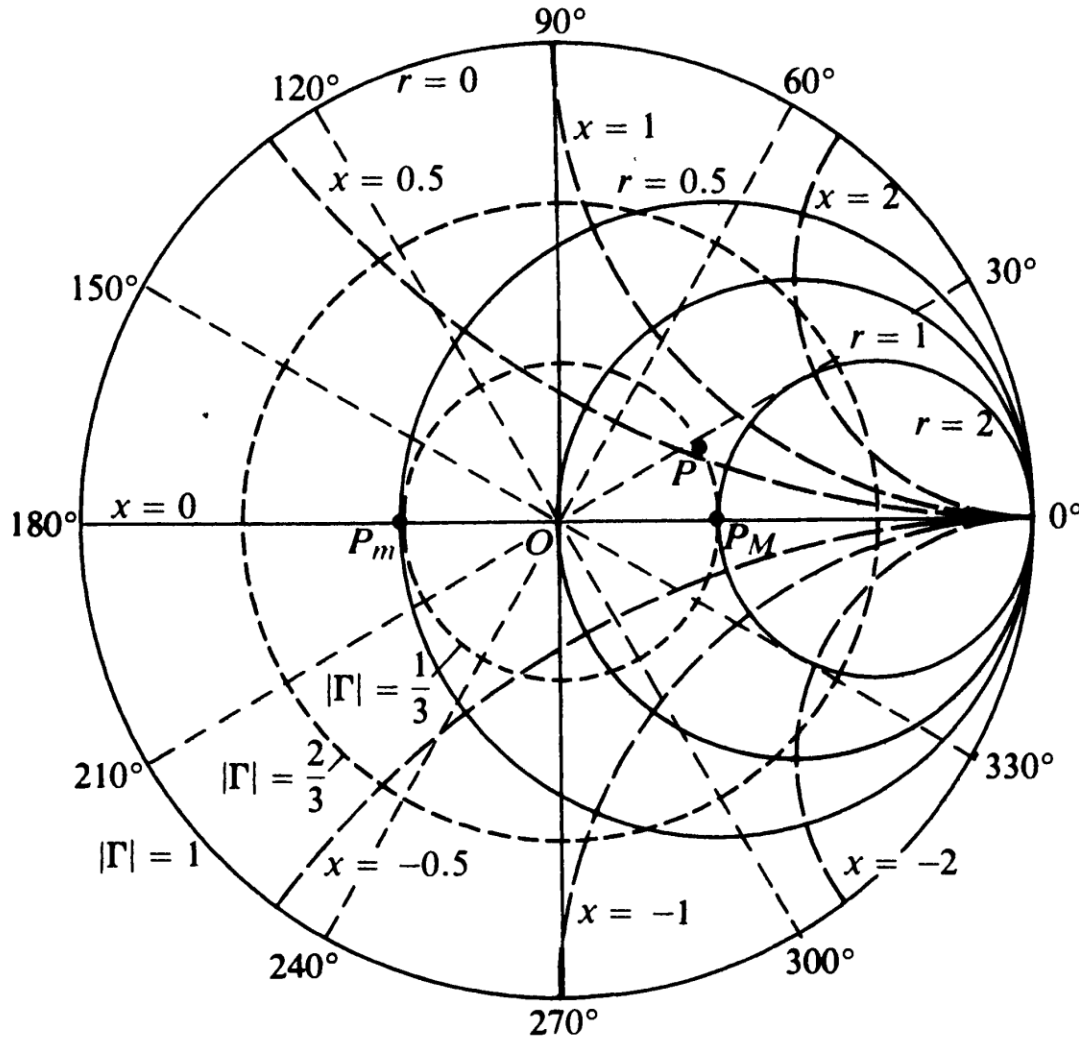


The intersection of an r -circle and an x -circle defines a point that represents a normalized load impedance

Important points about Smith chart

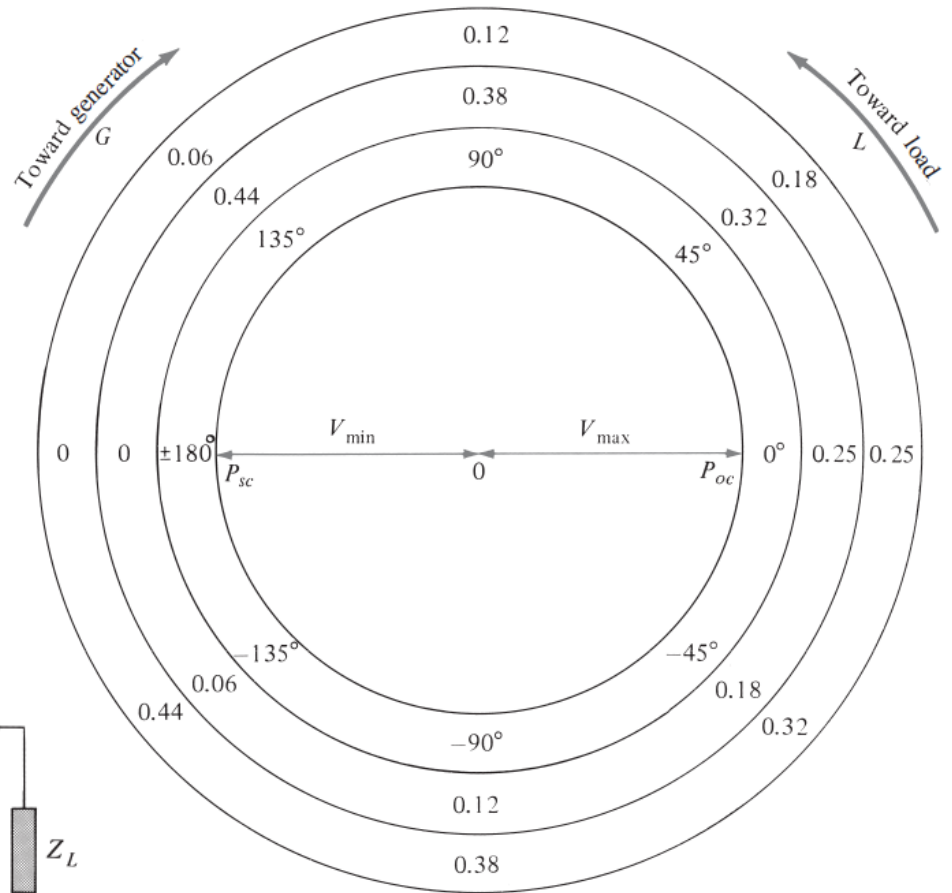


(a)

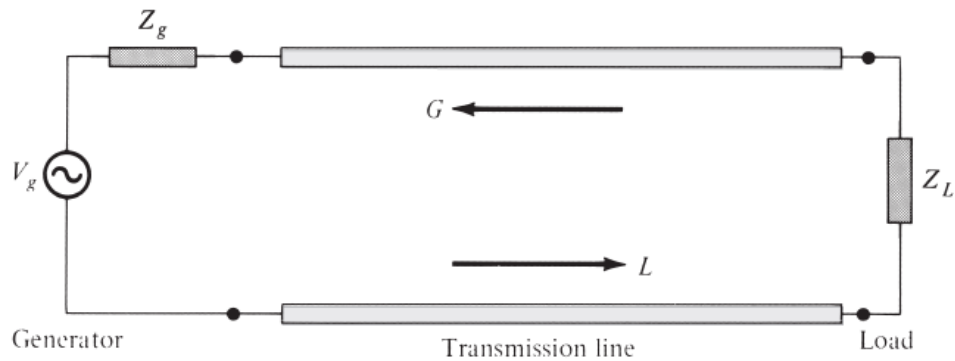

(b)

Lecture - 33

- Impedance divided by line impedance (50 Ohms)
 - $Z1 = 100 + j50$
 - $Z2 = 75 - j100$
 - $Z3 = j200$
 - $Z4 = 150$
 - $Z5 = \text{infinity}$ (an open circuit)
 - $Z6 = 0$ (a short circuit)
 - $Z7 = 50$
 - $Z8 = 184 - j900$
- Then, normalize and plot. The points are plotted as follows:
 - $z1 = 2 + j$
 - $z2 = 1.5 - j2$
 - $z3 = j4$
 - $z4 = 3$
 - $z5 = \text{infinity}$
 - $z6 = 0$
 - $z7 = 1$
 - $z8 = 3.68 - j18S$

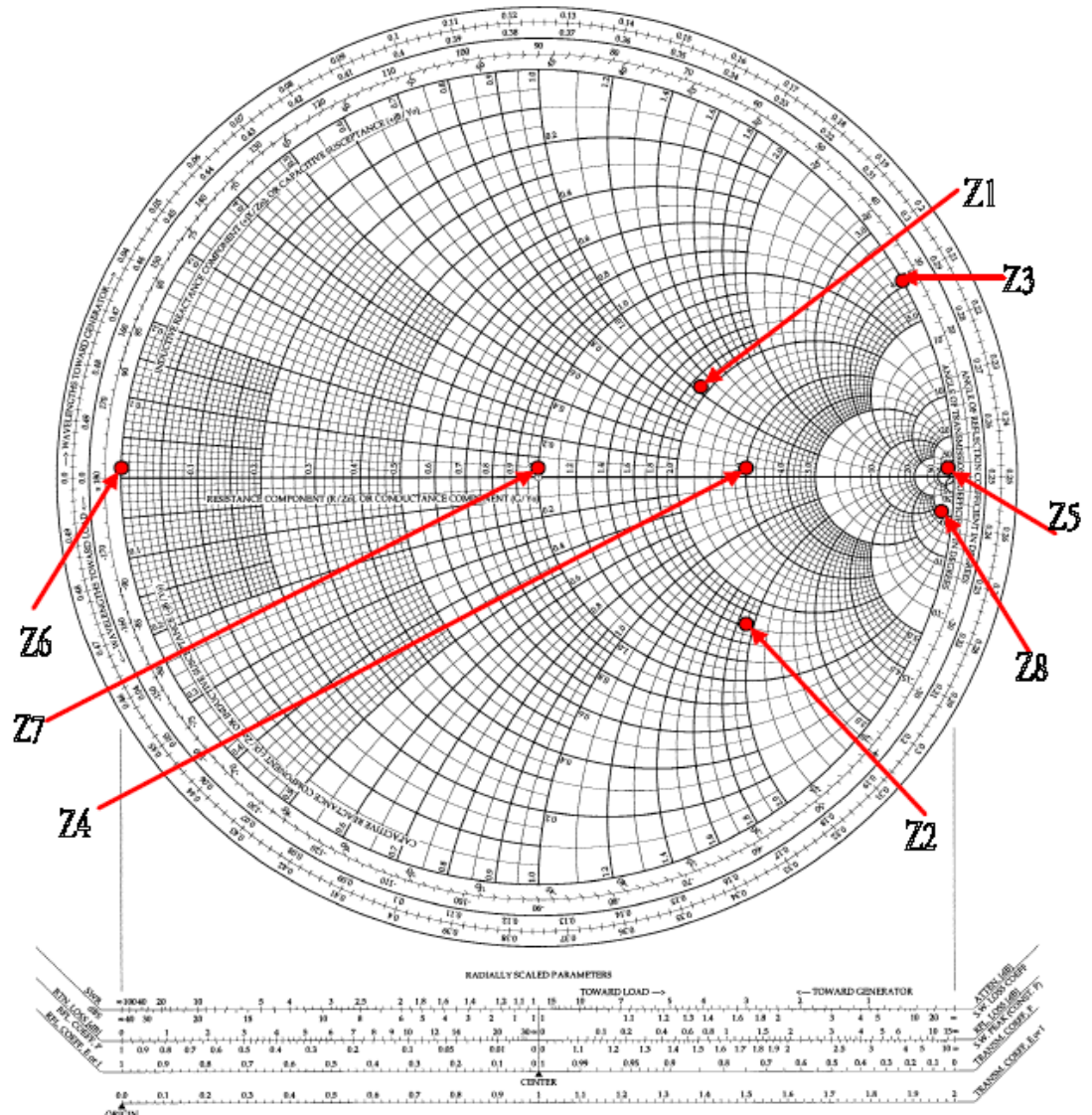

Plotting a constant VSWR circle

Step1: Locate the normalized load impedance on the chart (say P)

Toward Generator

Step3: The value of r at this point gives you SWR 's'

Constant VSWR Circle


Away From Generator

P

S value


O

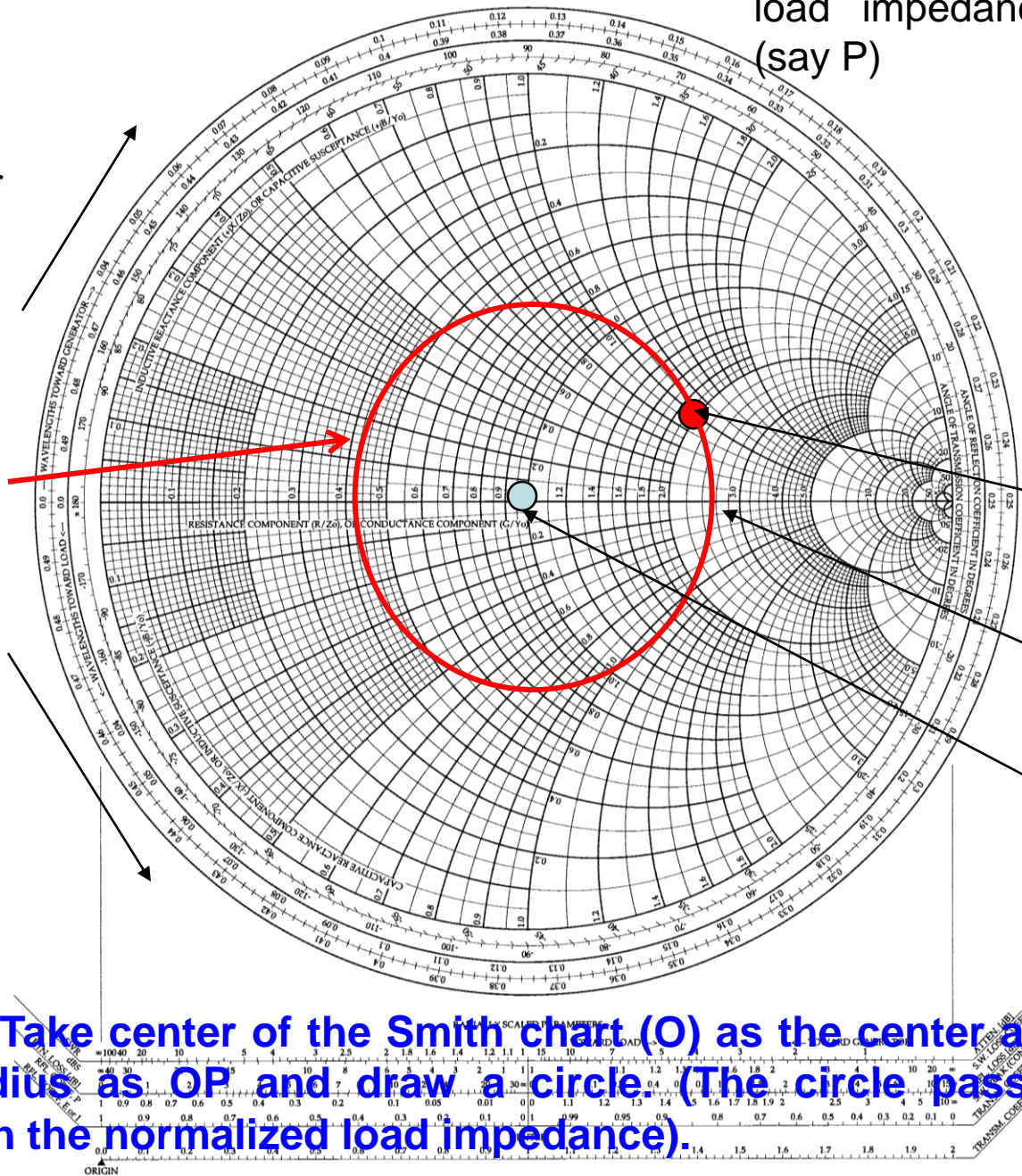Step2: Take center of the Smith chart (O) as the center and the radius as OP and draw a circle. (The circle passes through the normalized load impedance).



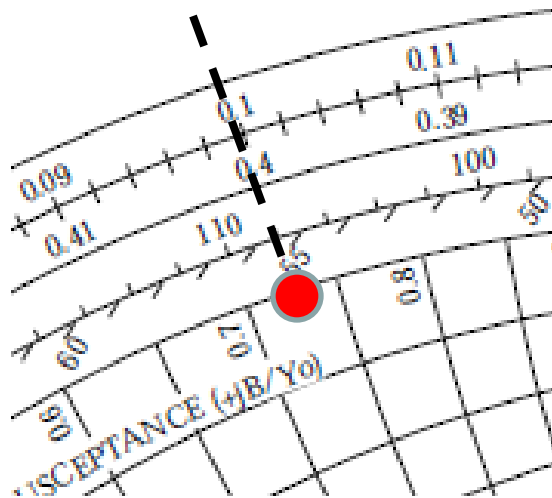Example

- Find the input impedance of a section of a $50\ \Omega$ loss-less transmission line that is 0.1λ long and is terminated in a short circuit.




Applications of Smith Chart

- **To find input impedance using a known load**
- Given that: $Z_L = 100-j50$ Ohm; $Z_o = 50$ Ohm; length of 0.1λ
- **Step1:** Find normalized impedance
- **Step2:** Locate r and x intersection Point
- **Step3:** Draw VSWR circle
- **Step4:** Extend the line OA at the end of chart and move 0.1λ towards generator.
- **Step5:** The line that intersect the VSWR circle gives point B.
- **Step6:** Find coordinates of B. This gives impedance at B (Z_B)
- **Step7:** Calculate $Z_{in} = Z_o Z_B = 30-j33$

Step4: Extend the line OA at the end of chart and move 0.1λ towards generator

Step3: Draw VSWR circle

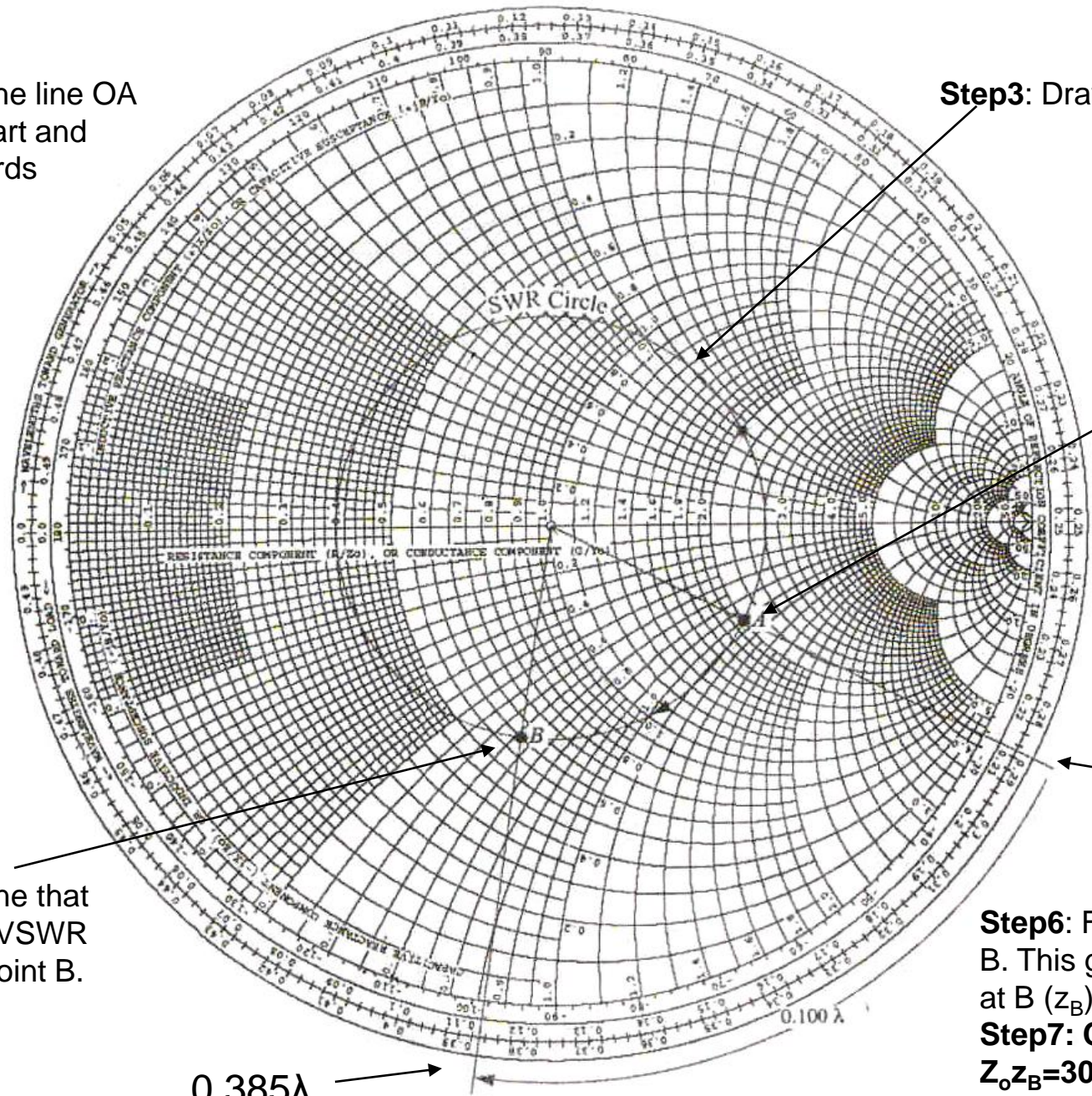Step1: Find normalized impedance
Step2: Locate r and x intersection Point



Step5: The line that intersect the VSWR circle gives point B.

Step6: Find coordinates of B. This gives impedance at B (z_B)
Step7: Calculate $Z_{in} = Z_0 z_B = 30 - j33$

To find the reflection coefficient for a known load

1. Normalization

$$\begin{aligned} z_n &= (25 + j\ 100)/50 \\ &= 0.5 + j\ 2.0 \end{aligned}$$

3. Find normalized reactance arc

$$x = 2.0$$

2. Find normalized resistance circle


$$r = 0.5$$

4. This vector represents the reflection coefficient

$$\Gamma = 0.52 + j0.64$$

$$|\Gamma| = 0.8246$$
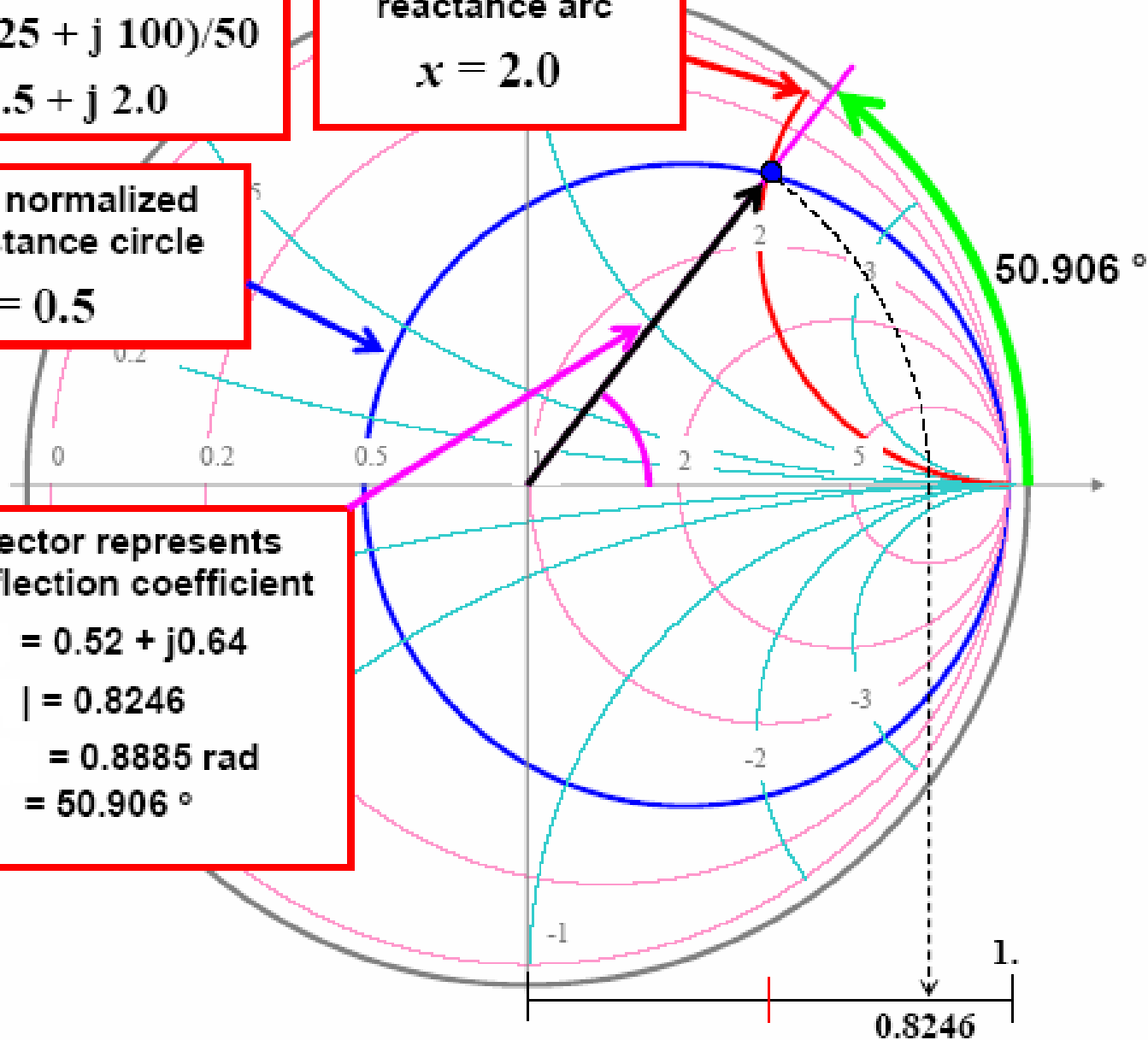
$$\begin{aligned} \angle \Gamma &= 0.8885 \text{ rad} \\ &= 50.906^\circ \end{aligned}$$



Lecture-34

To find the admittance for a known load

$$Z_L = 30 + j70$$


Step1:

Normalized
impedance

step2


Y_B

$$Y = Y_o Y_B = y_B / Z_o$$


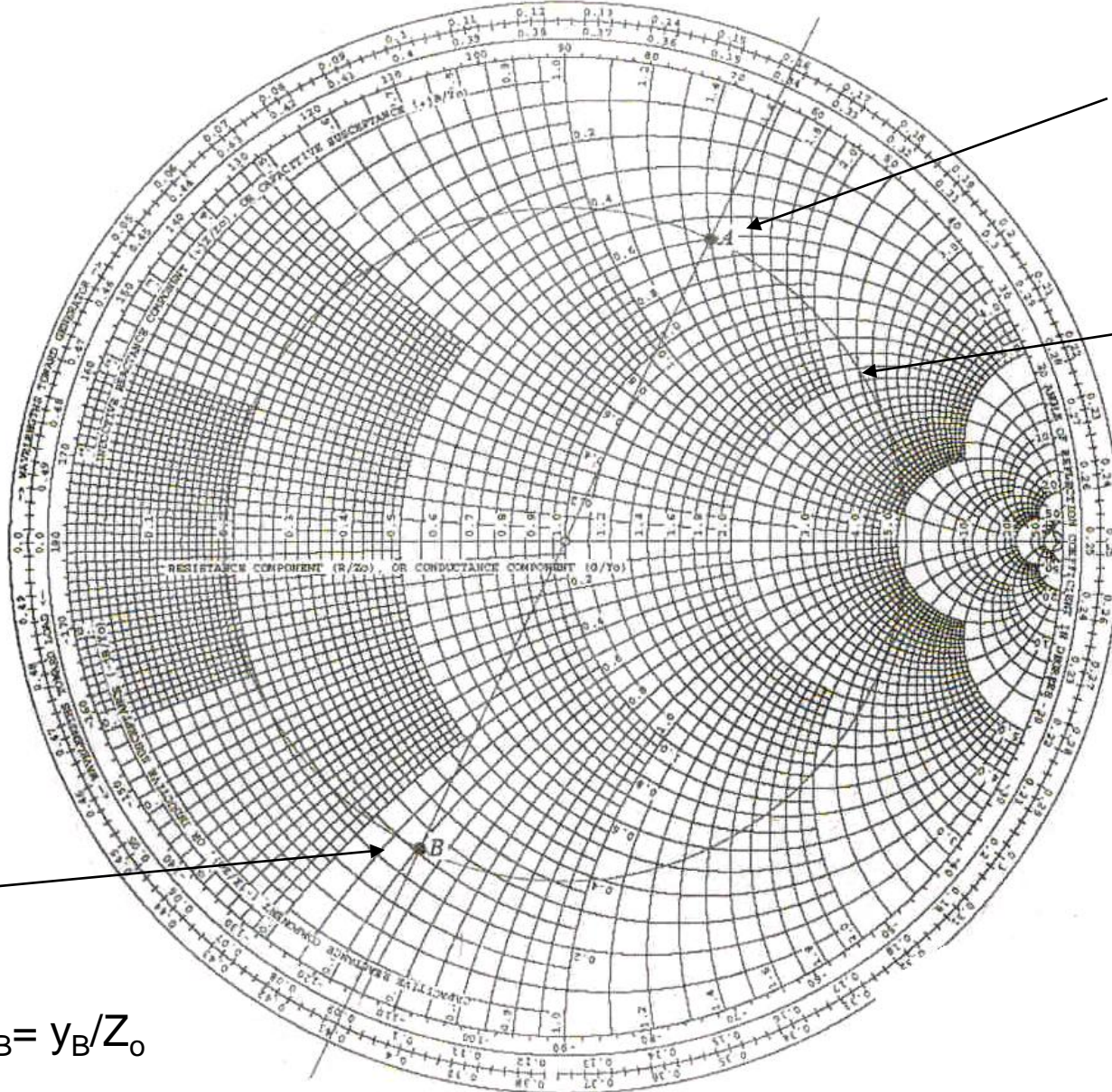


To find the location of V_{\max} and V_{\min} on a line from a known load

$$Z_L = 30 - j40 \text{ ohm}$$

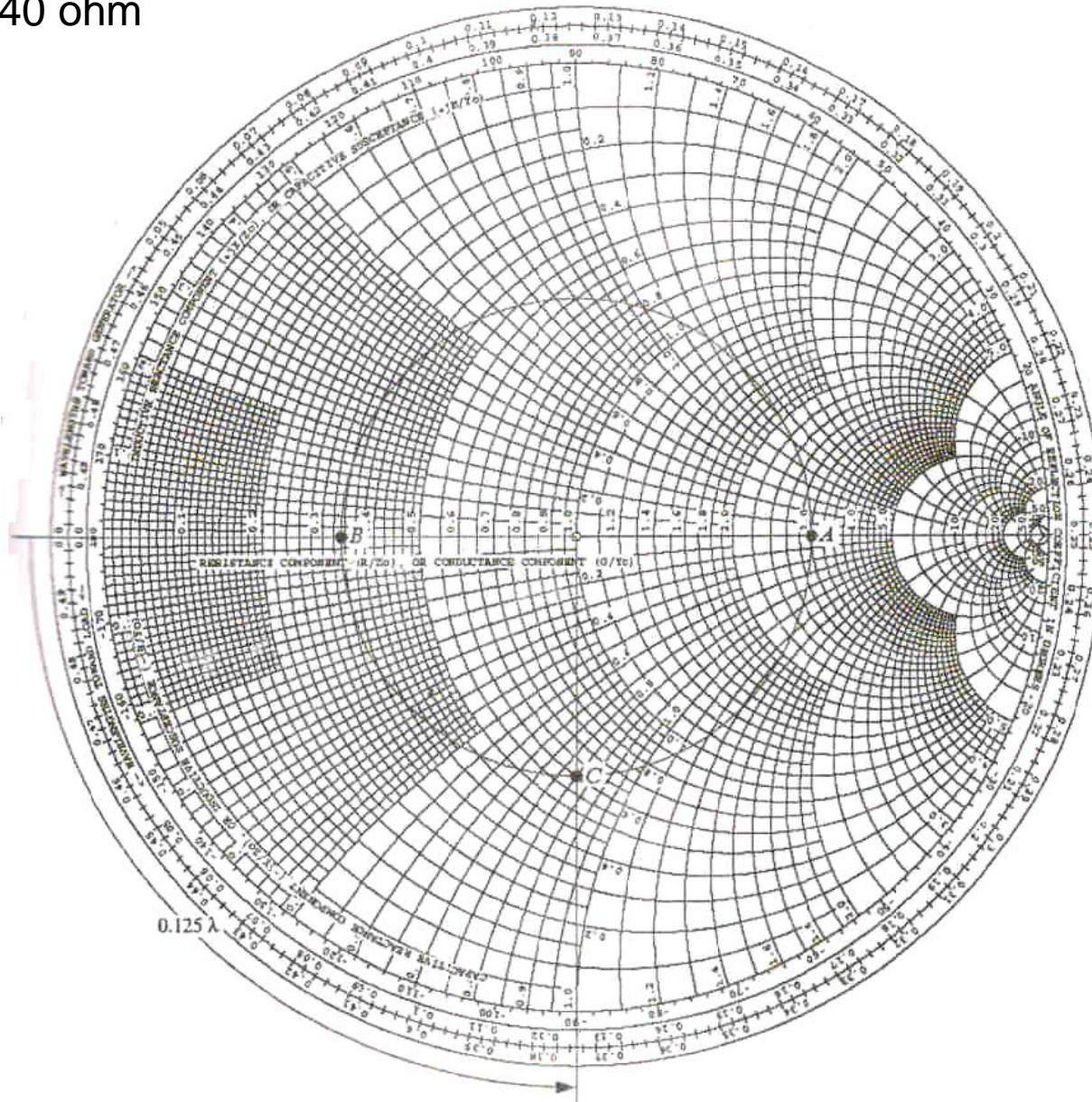


Maximum Power transfer to the Load

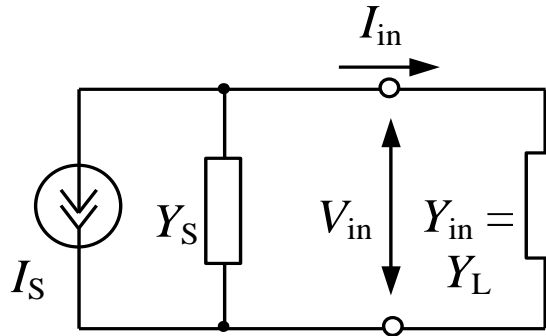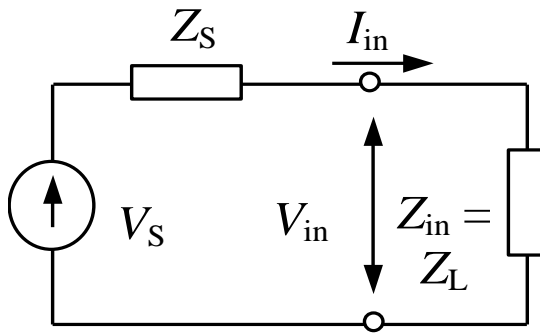

$Z_S = R_S + jX_S$ -
source impedance

$Z_L = R_L + jX_L$ -
load impedance

$$P = \frac{1}{2} V_{in}^2 \operatorname{Re} \left(\frac{1}{Z_L} \right) = \frac{1}{2} V_S^2 \left| \frac{Z_L}{Z_S + Z_L} \right|^2 \operatorname{Re} \left(\frac{1}{Z_L} \right) \quad \text{- power delivered to load}$$

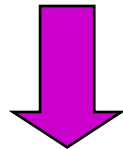


(substitution of real and imaginary
parts of source and load impedances)

$$P = \frac{1}{2} V_S^2 \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \quad \text{- power delivered to load as
function of circuit parameters}$$

For fixed source impedance Z_S , to maximize output power
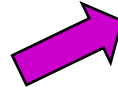
$$\frac{\partial P}{\partial R_L} = 0 \quad \frac{\partial P}{\partial X_L} = 0$$



$$\begin{cases} R_S^2 - R_L^2 + (X_L + X_S)^2 = 0 \\ X_L(X_L + X_S) = 0. \end{cases}$$



$$P = \frac{1}{2} V_S^2 \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$



$$P = \frac{V_S^2}{8R_S} \quad \text{- maximum power delivered to load}$$

$$\begin{cases} R_S = R_L \\ X_L = -X_S \end{cases} \quad Z_L = Z_S^*$$

- impedance conjugate matching conditions

$$\begin{cases} G_S = G_L \\ B_L = -B_S \end{cases} \quad \text{or} \quad Y_L = Y_S^*$$

- admittance conjugate matching conditions

Impedance Matching Techniques

Impedance matching is necessary to provide maximum delivery of RF power to load from source

Impedance matching using :

- Lumped elements
- **Quarter-Wave transformer**
- Single-Stub Tuner
- Double-Stub Tuner