

*Note: Attempt all parts of a question together*

Q1. (a) For the Boolean expression given below

$$F(A,B,C,D) = \Sigma (0,1,2,5,6,7)$$

$$d(A,B,C,D) = \Sigma (8,9,10,11,12,14,15)$$

- (i) Plot the k-Map
- (ii) Identify the Prime Implicants. Express each PI as product form.
- (iii) Identify the essential Prime Implicants. Express each EPI as product form.
- (iv) How many different minimal SOPs are possible for F and write down the expression for all the possible expressions.

(b) Find the complement of  $F(A,B,C,D) = AB + ((BC)'(A+D)')$

[22+5]

Q2. (a) Implement the function  $F(A,B,C,D,E) = A'B'C'DE' + ABCD'E$  only using the required components from the following list:

1. 3:8 decoder with active high outputs and an active high enable input -1 No.
2. 8:3 Priority Encoder with input no. 7 at highest priority with one active high enable which if disabled forces the outputs to logic low – 1 No.
3. 2 input XOR gate – 1 No., 2 input OR gate – 1 No., 2 input AND gate – 1 No.

(b) Design a digital circuit which has a three bit input  $A_2A_1A_0$  and three bit output  $Y_2Y_1Y_0$  to perform the following function:

The circuit takes the input  $A_2A_1A_0$  and produces the one's complement of the input number. This is followed by producing the Gray code of the ones complement output. The gray code is the final output,  $Y_2Y_1Y_0$ , of the circuit.

Design the circuit only using not more than 5nos of 2:1 MUXs.


[14+14]

Q3. (a) Construct the following using D Flip Flops and basic logic gates:

- (i) T Flip Flop
- (ii) JK Flip Flop

(b) Identify the function implemented by the circuit using transmission gates and inverters as shown below. Write the characteristic table and characteristic equation for the function.


[10+13]

 

 Q4. (a) For the TTL circuit shown in figure:

- Find the logical function of the gate and the states of all transistors and diodes for all input combinations.
- Find  $V_{OL}$ ,  $V_{IL}$ ,  $V_{IH}$  and low state noise margin.

Given:  $V_{BE(ON)} = 0.7\text{ V}$ ,  $V_{BE(SAT)} = 0.8\text{ V}$ ,  $V_{CE(SAT)} = 0.2\text{ V}$ ,  $V_{BE(OFF/REV)} = V_{D(OFF/REV)} = 0.5\text{ V}$ ,  $V_{D(ON)} = V_{BC(ON)} = 0.7\text{ V}$



Q4 (b) Implement the following Boolean function using CMOS logic using minimum no of MOS Transistors.

$$Y = (F [A(B + DE) + C (E + BD)])$$

[10+12]